

Electrical Circuits and Logic

Text Chapter 3 – Section 7

Proposition – Electrical Switch

- A proposition is true or false, not both.
- An electric switch is on or off, not both.
- If a switch is open (off) the power can not pass through.
- If a switch is closed (on) the power will pass through.

No in-class assignment problem


Electrical Circuits – Logical Statements

- Switch on(closed)will be represented by T.
- Switch off (open) will be represented by F.
- A TV is plugged into a wall outlet governed by a switch.
- The TV has an on-off button.
- The TV will be on only if both the wall switch and the on-off button the TV are on.
- Let wall switch be p and the on-off switch be q.

No in-class assignment problem

Series – One path for power

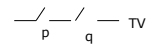- This type of circuit is called a series.
- A series circuit may be logically represented as a conjunction.
- TV on only if both are on.
- Series ↔ Conjunction




p	q	TV	$p \wedge q$
T	T	T - on	T
T	F	F - off	F
F	T	F - off	F
F	F	F - off	F

No in-class assignment problem

Parallel – 2 or more paths for power

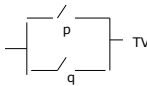- In this case the power can flow through either path or both.
- A parallel circuit can be logically represented as a disjunction.
- Parallel → Disjunction.




p	q	TV	$p \vee q$
T	T	T - on	T
T	F	T - on	T
F	T	T - on	T
F	F	F - off	F

No in-class assignment

A Switching Circuit as a Symbolic Statement

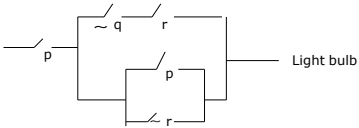1. Can the power go through more than one path? – parallel - or
2. In some parts can the power only go through one part? – series - and



No in-class assignment

The Symbolic Statement

- Write the symbolic statement.
- Make a truth table to determine under what conditions the light bulb will go on.

$$p \wedge [\sim q \wedge r \vee p \vee \sim r]$$

In-class Assignment 15 - 1

The Truth Table for the Circuit

$$p \wedge [\sim q \wedge r \vee p \vee \sim r]$$

P	q	r	$\sim q$	$\sim r$	1 $\sim q \wedge r$	2 $p \vee \sim r$	$1 \vee 2$	$p \wedge (1 \vee 2)$
T	T	T	F	F	F	T	T	T
T	T	F	F	T	F	T	T	T
T	F	T	T	F	T	T	T	T
T	F	F	T	T	F	T	T	T
F	T	T	F	F	F	F	F	F
F	T	F	F	T	F	T	T	F
F	F	T	T	F	T	F	T	F
F	F	F	T	T	F	T	T	F

In-class Assignment 15 - 2

Drawing an Electrical Circuit from a Symbolic Statement


- Note the conjunctions which mean these switches will be connected in series (in the same line).
- Note the disjunctions which these switches will be connected in parallel (different lines),

$$p \vee \sim r \wedge r \vee q$$

In-class Assignment 15 - 3

The Switching Circuit

$$p \vee \sim r \wedge r \vee q$$

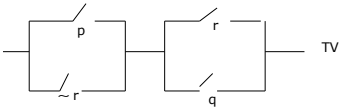

In-class Assignment 15 - 3